
Hand In 4

FYST85

Author

Max Eriksson

maxerikss@gmail.com

Lund University

Department of Physics



LUND
UNIVERSITY

November 25, 2024

1 First Exercise


Firstly the NAND-gate looks like



A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Figure 1: NAND-gate and the corresponding truth table.


Now we can easily make the AND-gate

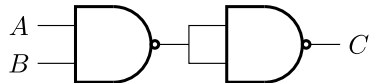

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Figure 2: AND-gate and the corresponding truth table.


As well as the NOT-gate

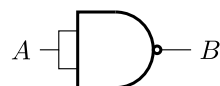

A	B
0	1
1	0

Figure 3: AND-gate and the corresponding truth table.

And finally the XOR-gate

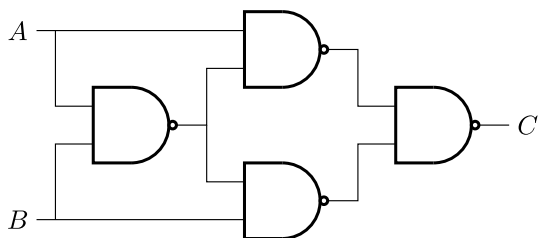

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

Figure 4: XOR-gate and the corresponding truth table.

2 Second Exercise